



Multi-phase Clock Generator for High-speed Wireline Systems

Shaokang Zhao

Supervisor: Prof. C. Patrick Yue

25th March 2025

Optical Wireless Lab

Department of Electronic and Computer Engineering

The Hong Kong University of Science and Technology (HKUST)

Outline


- Introduction
- Clocking in Wireline Systems
- Proposed QCG with Open-loop QEC
- Measurement Results
- Conclusion and Future Work

Outline

- Introduction
- Clocking in Wireline Systems
- Proposed QCG with Open-loop QEC
- Measurement Results
- Conclusion and Future Work

Introduction: Background

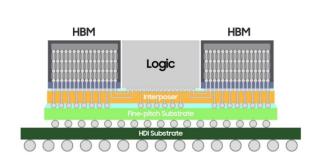
- We are now in an era of artificial intelligence (AI)
- Hardware to support AI:
 - High performance computing (HPC) systems
 - High performance data transmission



High-bandwidth Memory IO (Chip-to-memory)



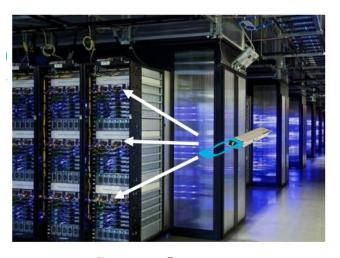
PCIE, NVLink (Inter-component, chip-to-chip)



Data Center (Server-to-server)

Introduction: Wireline Transceivers

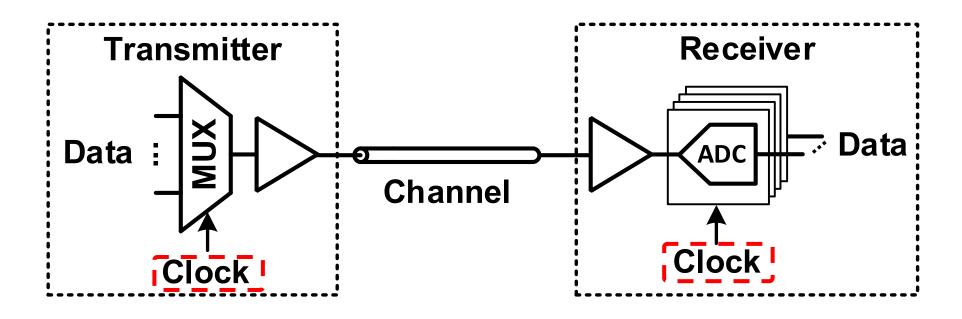
- Wireline transceivers: transmitter (TX), channel, and receiver (RX)
- Clock signal plays an important role in providing synchronization and supporting various functionalities




Outline

- Introduction
- Clocking in Wireline Systems
 - Clocking architectures
 - Review on QCG circuits
- Proposed QCG with Open-loop QEC
- Measurement Results
- Conclusion and Future Work

Clocking architecture

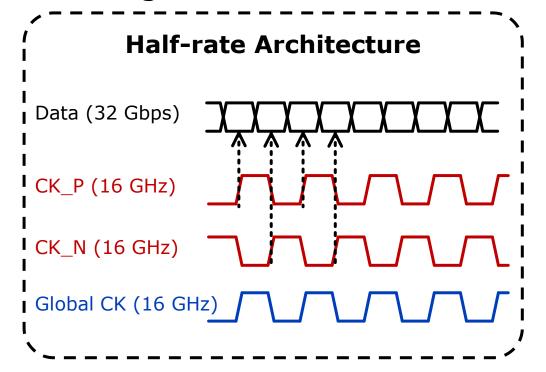

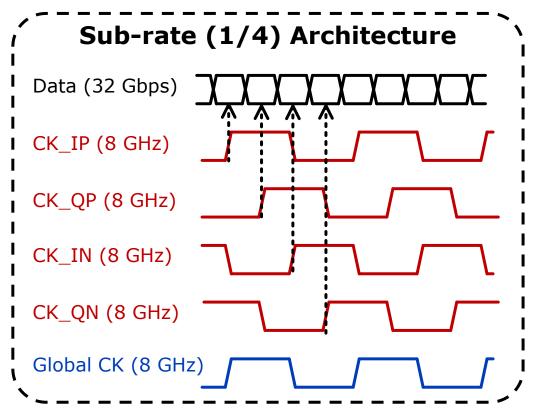- Straightforward implementation
- High-power clock generation and distribution
- Bandwidth issue for clock buffers




- Relieved power and bandwidth issue
- Requires multi-phase sampling clocks

Quadrature clock generation (QCG): generating 4-phase clocks from differential clocks with:

- High phase accuracy (duty cycle = 50%, quadrature phase = 90°)


 Least jitter contribution CK_1P **CK 1N** QCG CK_1P (0°) CK_1N (180°) CK_IP **QCG CK QP (90°** CK_QP CK_IN **CK_IP** (0°) **CK_IN (180°)** CK_QN CK QN (90°)

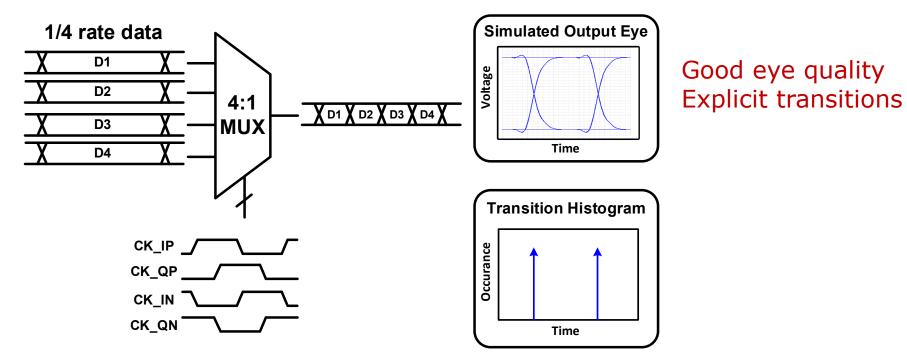- Requirements for quadrature clocks:
 - − Jitter ~ system random jitter (RJ)
 - − Phase error ~ system deterministic jitter (DJ)



A quarter-rate wireline transmitter using: (a) Ideal 4-phase sampling clocks

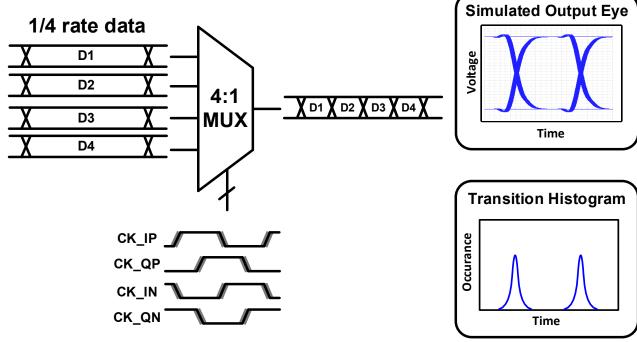- Requirements for quadrature clocks:
 - − Jitter ~ system random jitter (RJ)
 - Phase error ~ system deterministic jitter (DJ)




J

Degraded eye quality

Transitions blurred/distributed


A quarter-rate wireline transmitter using: (b) 4-phase sampling clocks with jitter

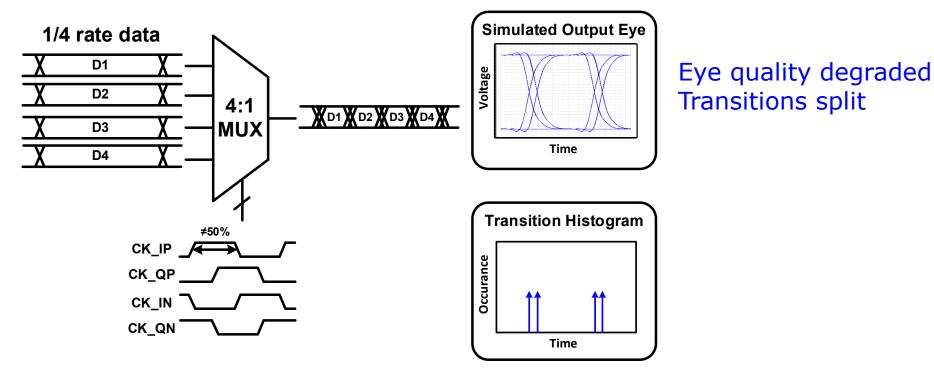- Requirements for quadrature clocks:
 - Jitter ∼ system random jitter (RJ)
 - − Phase error ~ system deterministic jitter (DJ)




A quarter-rate wireline transmitter using: (c) 4-phase sampling clocks with phase error-1

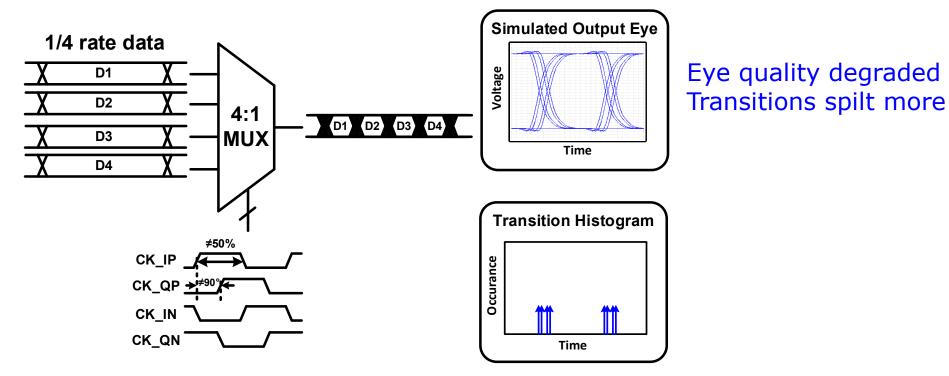- Requirements for quadrature clocks:
 - − Jitter ~ system random jitter (RJ)
 - − Phase error ~ system deterministic jitter (DJ)



A quarter-rate wireline transmitter using: (d) 4-phase sampling clocks with phase error-2

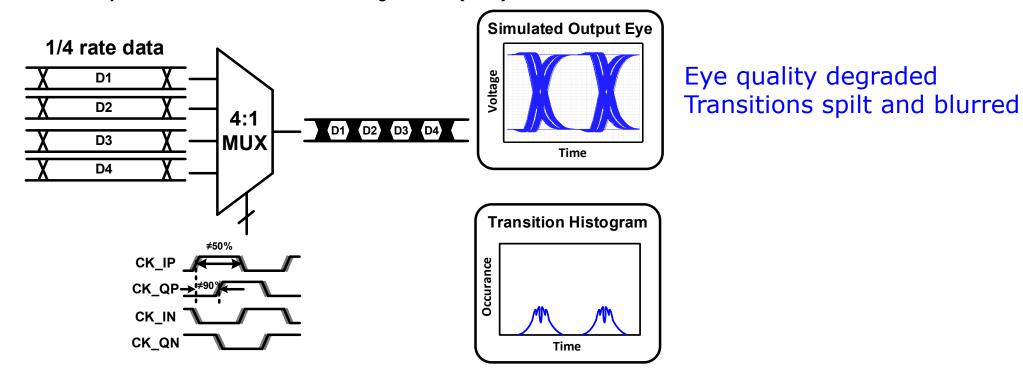
- Requirements for quadrature clocks:
 - − Jitter ~ system random jitter (RJ)
 - − Phase error ~ system deterministic jitter (DJ)



A quarter-rate wireline transmitter using: (e) 4-phase sampling clocks with both jitter and phase error


Review on QCG Circuits: Frequency divider

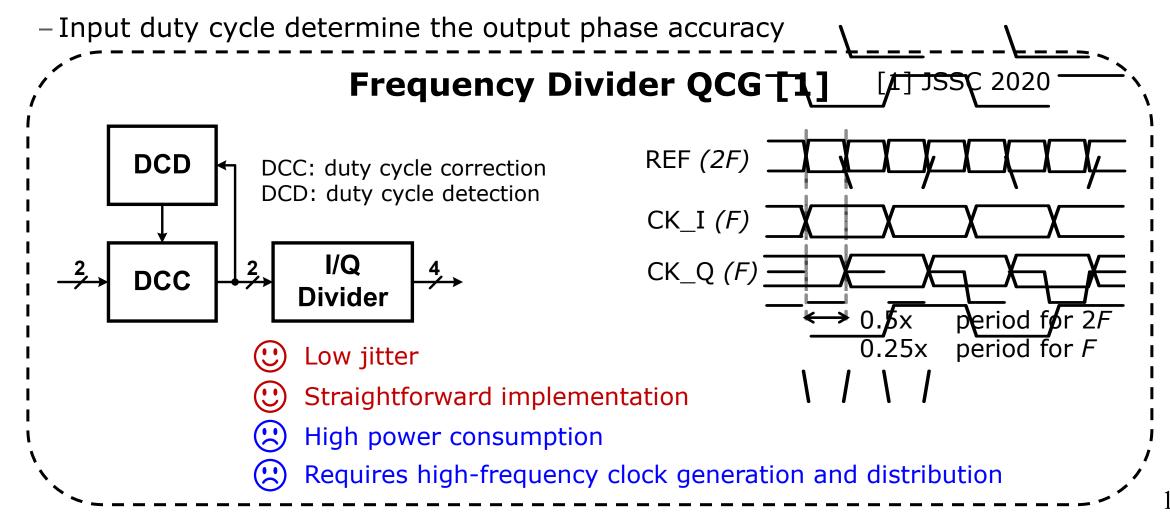Frequency divider: most commonly used QCG



Review on QCG Circuits: Delay-Locked Loop


Delay-locked Loop (DLL)

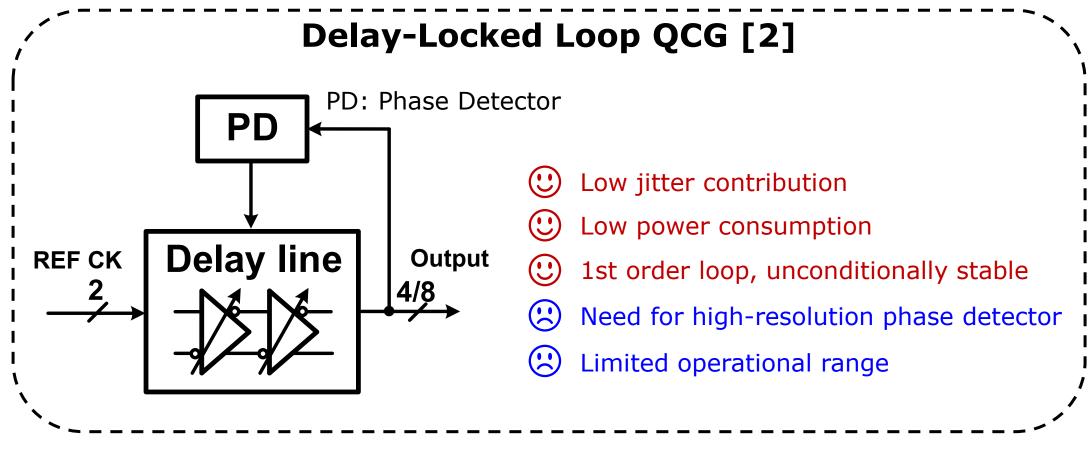

[2] ISSCC 2022

Review on QCG Circuits: Ring Oscillator

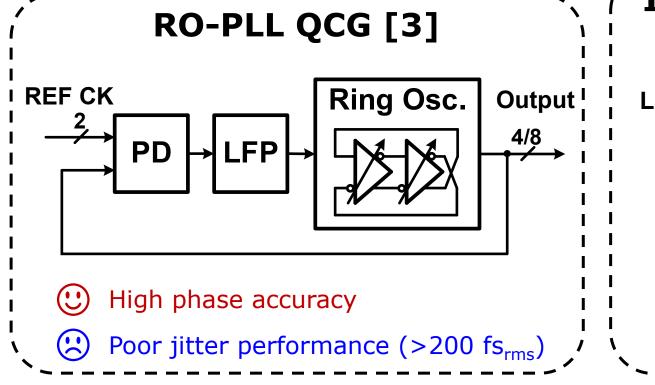- Ring-oscillator-based QCG
 - Ring oscillator phase-locked loop (RO-PLL)
 - Injection-locked ring oscillator




Injection-Locked RO QCG [4] RO stage #1 Low-noise 2 **Output** Improved jitter performance Open-loop, simple implementation Poor phase accuracy Sensitive to mismatch, losing lock

Outline

- Introduction
- Clocking in Wireline Systems
- Proposed QCG with Open-loop QEC
- Measurement Results
- Conclusion and Future Work

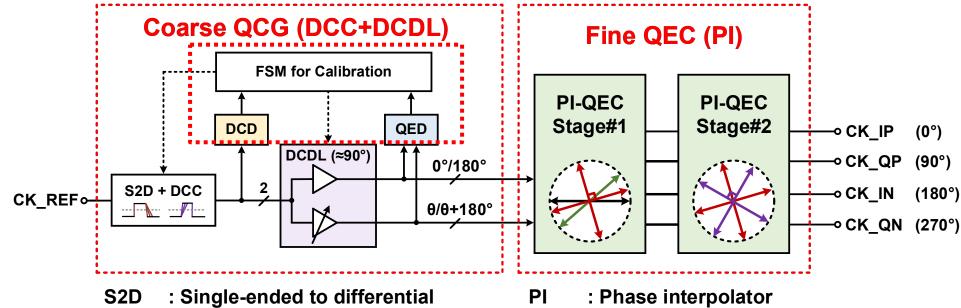- Proposed QCG:
 - Duty cycle correction (DCC)
 - A digital controlled delay line (DCDL)
 - A 2-stage open-loop quadrature error corrector (QEC)
 - FSM for automatic calibration




DCC: Duty cycle correction

DCDL : Delay line, generating θ≈90°

QEC : Quadrature error correction

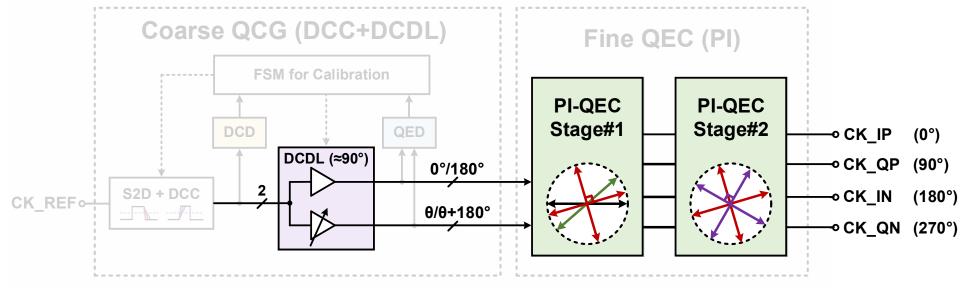- Proposed QCG:
 - Duty cycle correction (DCC)
 - A digital controlled delay line (DCDL)
 - A 2-stage open-loop quadrature error corrector (QEC)
 - FSM for automatic calibration




S2D : Single-ended to differential


DCC: Duty cycle correction


DCDL : Delay line, generating θ≈90°


PI : Phase interpolator


QEC: Quadrature error correction

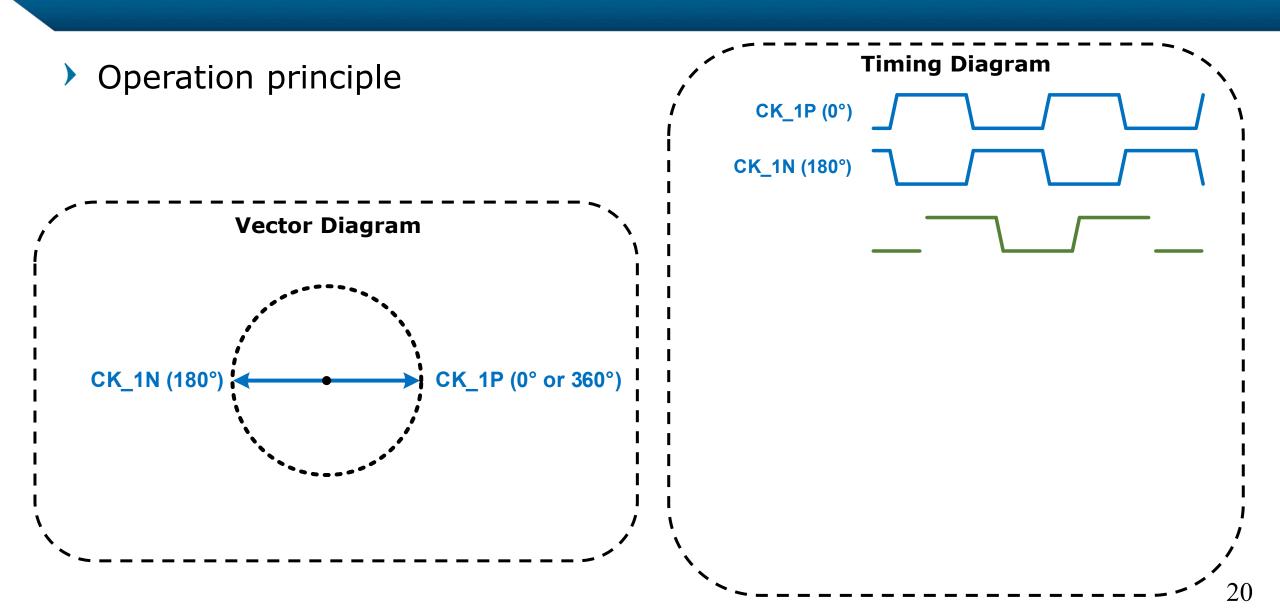

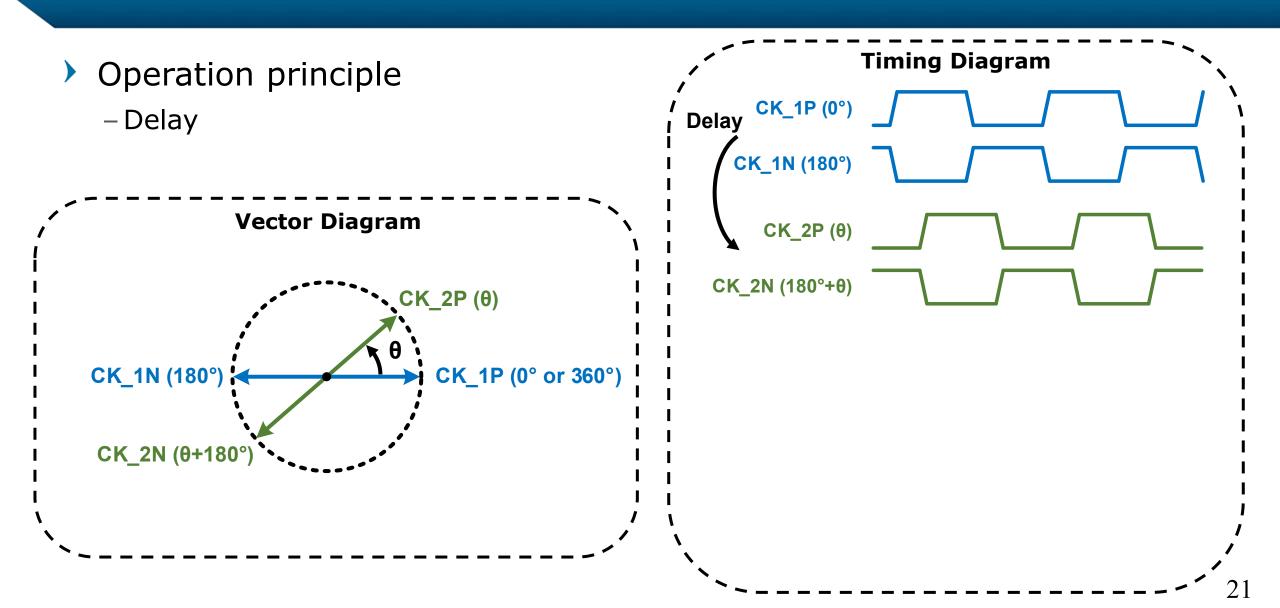

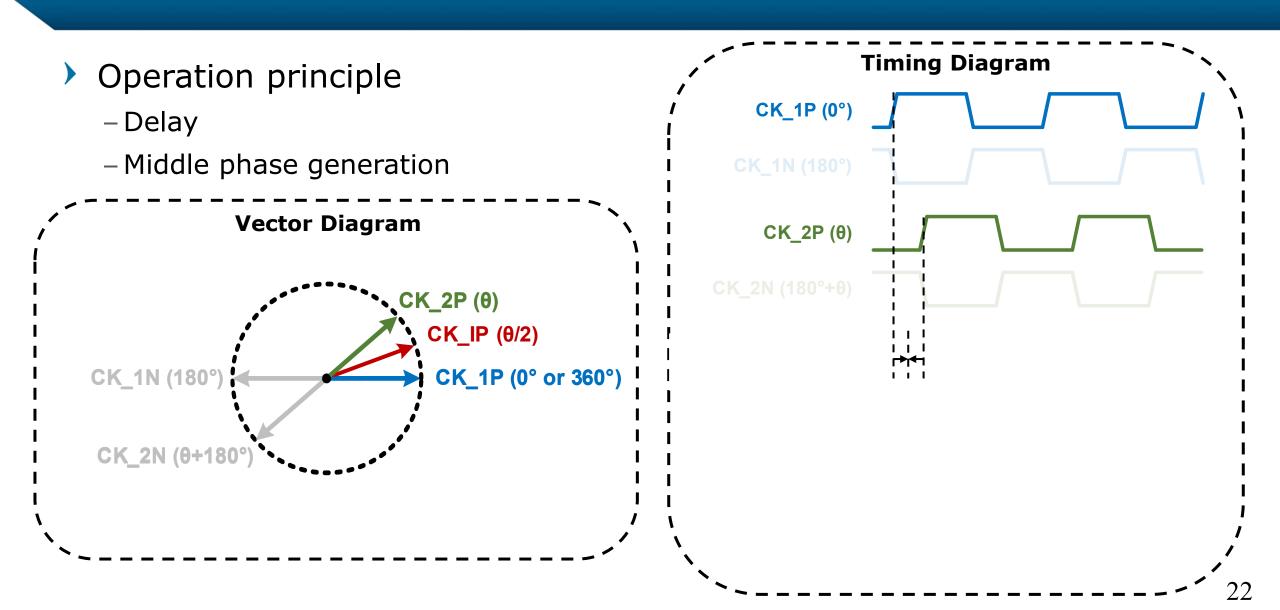


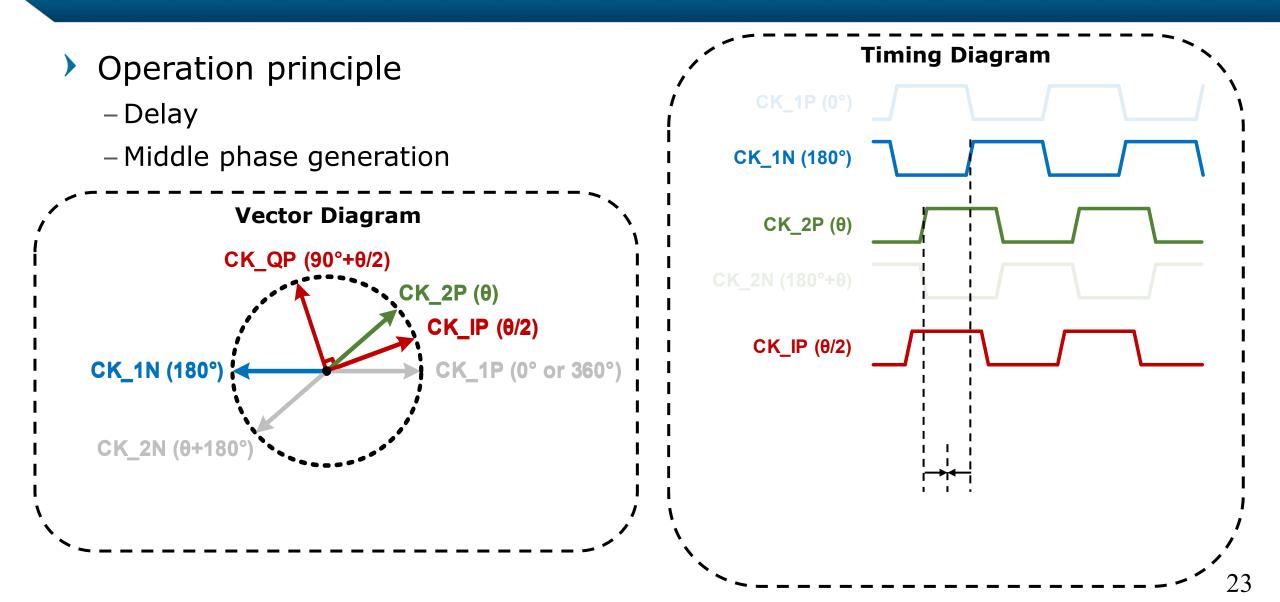


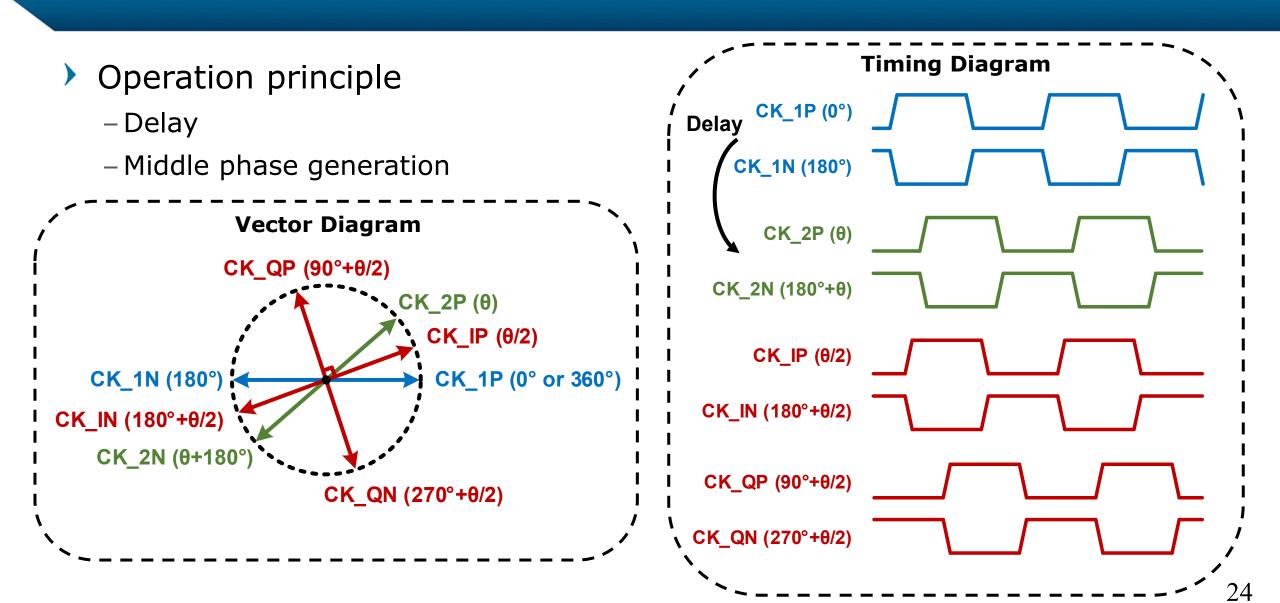

Proposed QCG: Circuit Implementation

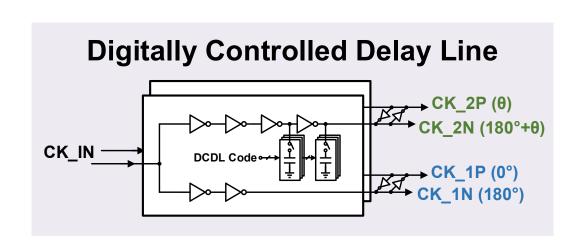
- Circuit implementation
 - A digitally controlled delay line (DCDL) generates coarse quadrature phase shift $(\theta \approx 90^{\circ})$
 - Phase interpolators (PI) produce middle phase



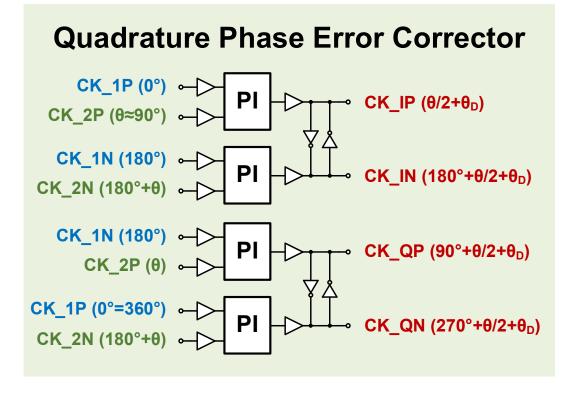


Proposed QCG: Choice of Phase Interpolator

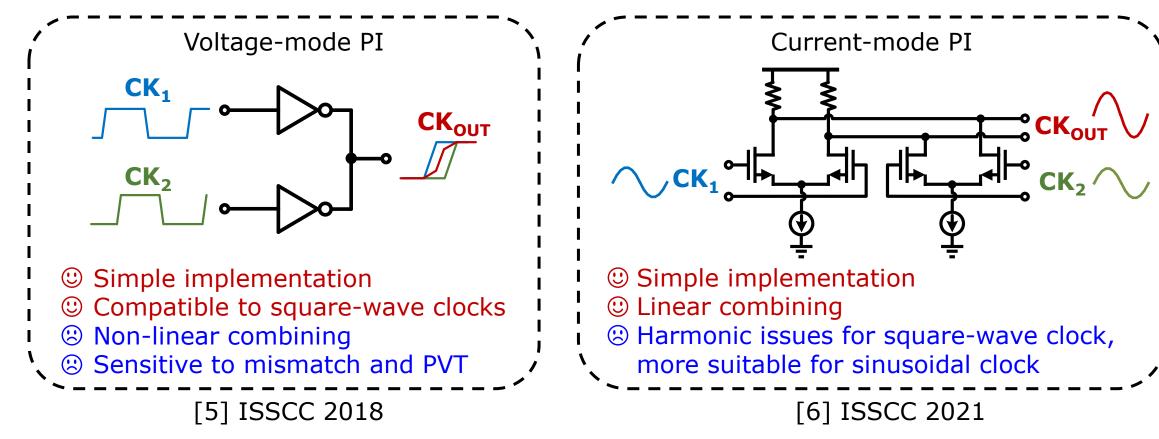- Commonly used PI
 - Voltage-mode PI: "wire-and" inverters
 - Current-mode PI: current-mode logic (CML) combiner



Proposed QCG: Choice of Phase Interpolator

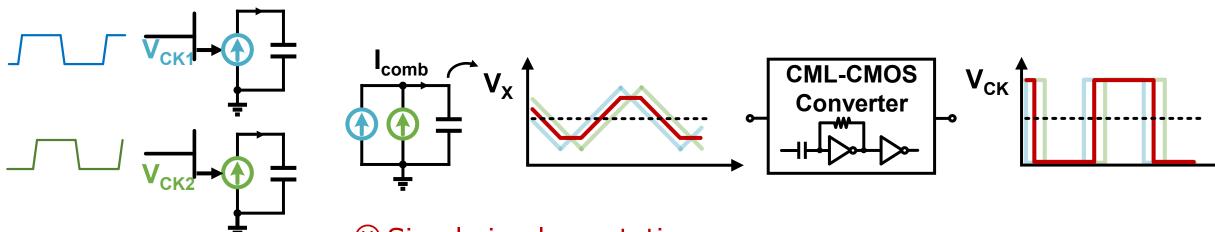
- Commonly used PI
 - Voltage-mode PI: "wire-and" inverters
 - Current-mode PI: current-mode logic (CML) combiner
- Integrating-mode PI (IMPI) [7, ISSCC 2021]




- Simple implementation
- © Linear combining
- © Compatible to square-wave clocks

Proposed QCG: Choice of Phase Interpolator

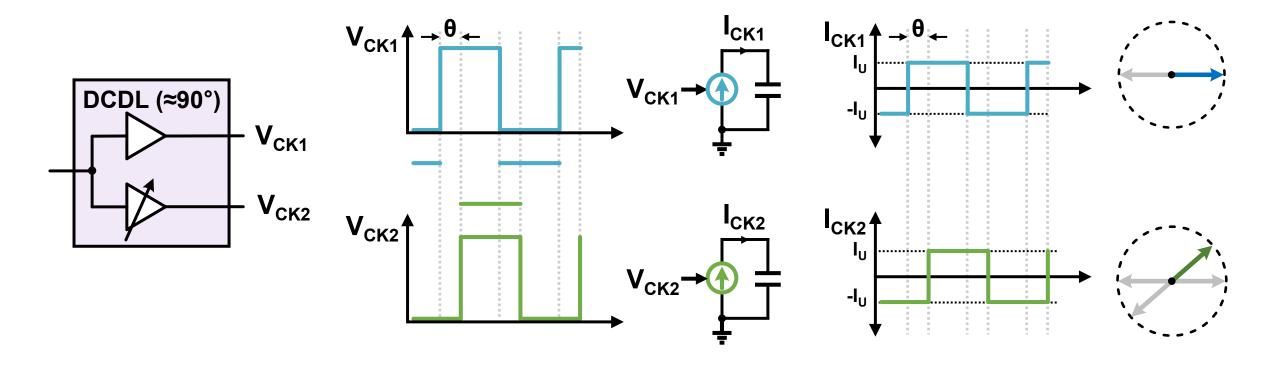
- Operation principle of integrating-mode PI
 - Converting voltage clocks to current clocks



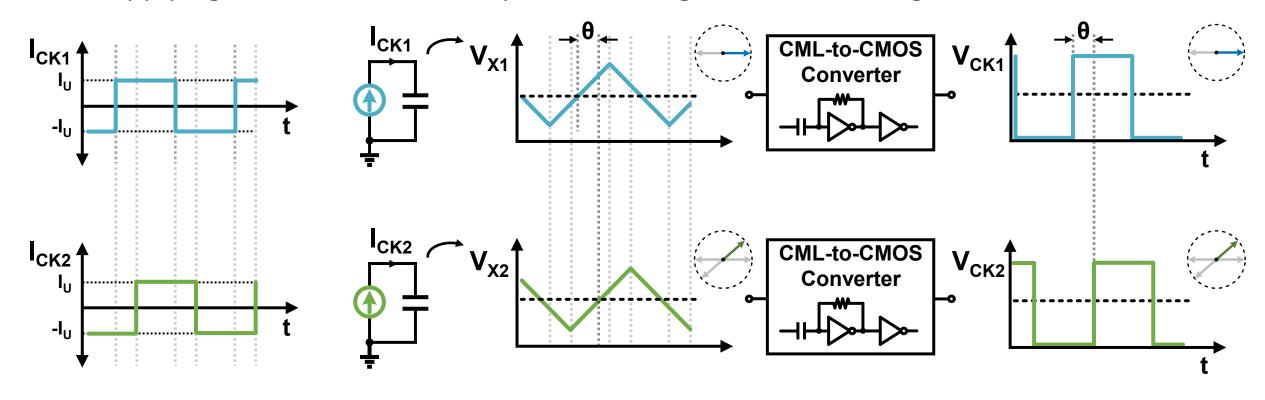
- Operation principle of integrating-mode PI
 - Applying current on a load capacitor: triangular waveforms generated



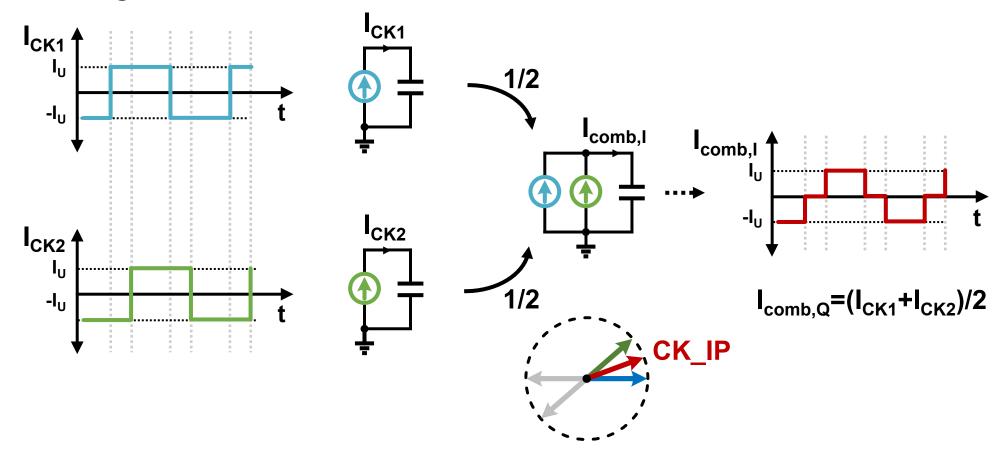
- Operation principle of integrating-mode PI
 - Combining the CK1 and CK2 currents



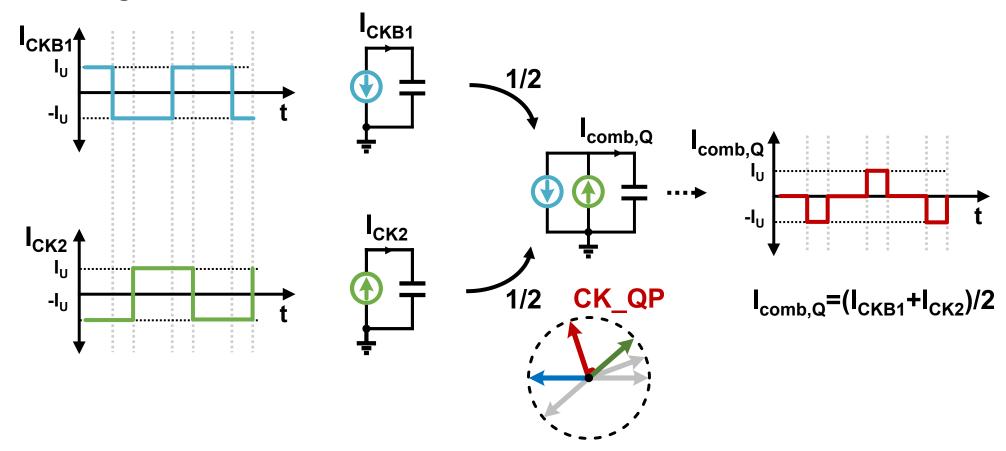- Operation principle of integrating-mode PI
 - Combining the CKB1 and CK2 currents




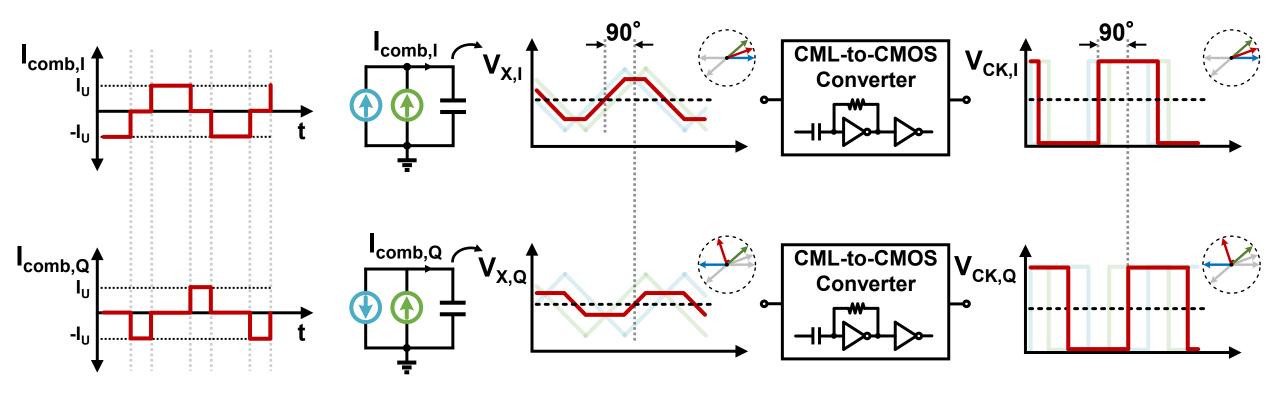- Operation principal of integrating-mode PI
 - Applying combined current clock on a load capacitor: trapezoidal waveforms generated




Proposed QCG: PI Circuit Implementation

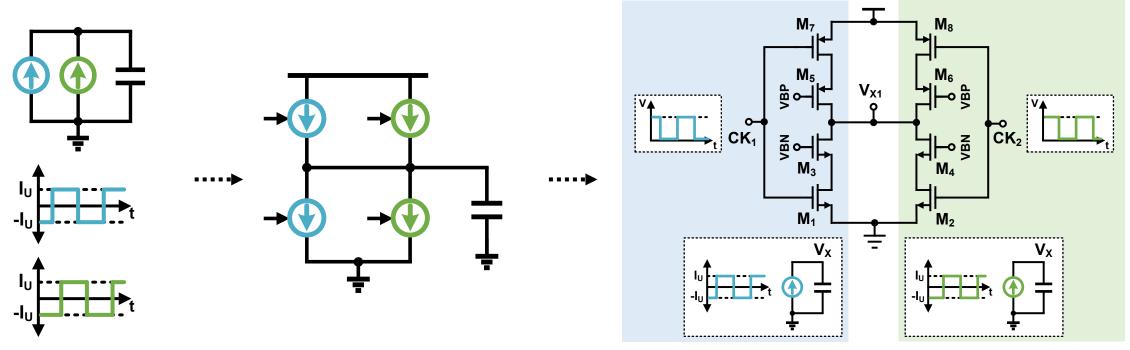- Current sources with charging and discharging phase
- Circuit implementation of integrating-mode PI
 - Charging: PMOS, discharging: NMOS
 - C²MOS logic to enable PMOS or NMOS at the pace of input clock




Proposed QCG: Two-stage QEC

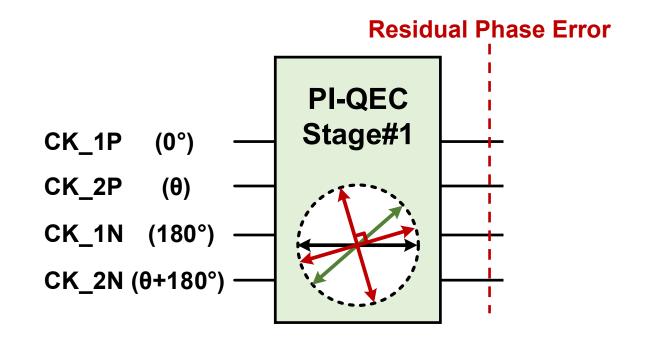
- Residual errors might exist after 1-stage open-loop QEC
- Additional stages can further reduce the errors
 - 2-stage QEC: considering noise and mismatch



Proposed QCG: QCG Performance

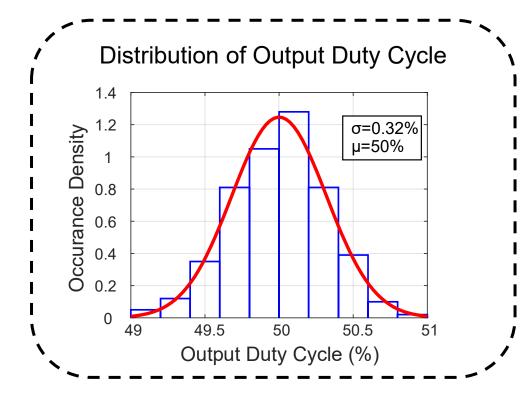
- > 500-run Monte Carlo simulation is performed to evaluate 2-stage QEC performance under mismatch
 - Duty cycle: μ =50%, σ =0.32%
 - Quadrature phase: μ =90.04°, σ =0.75°



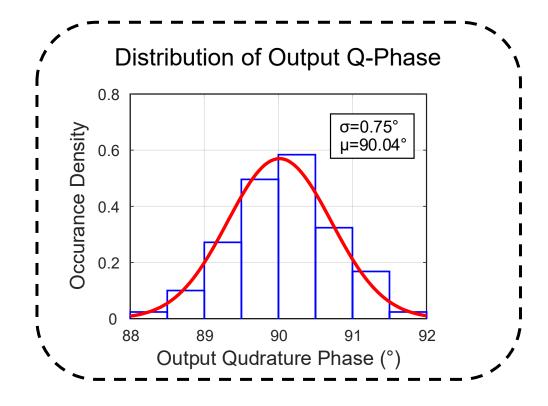


: Delay line, generating θ≈90°

Is it good enough?

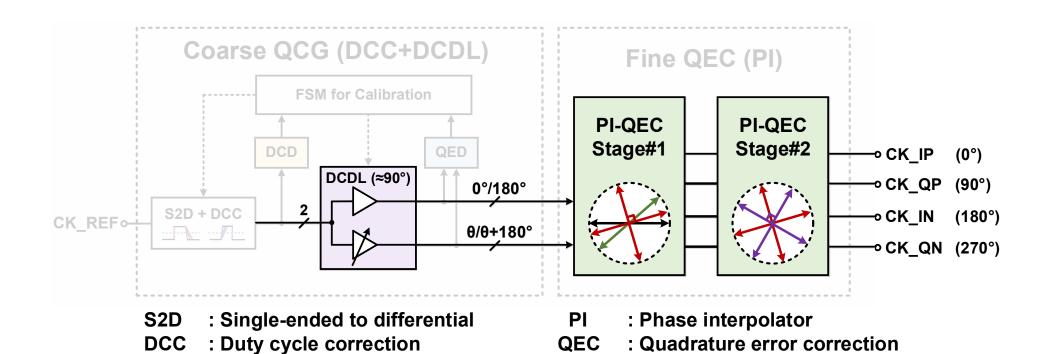


Proposed QCG with Open-loop QEC

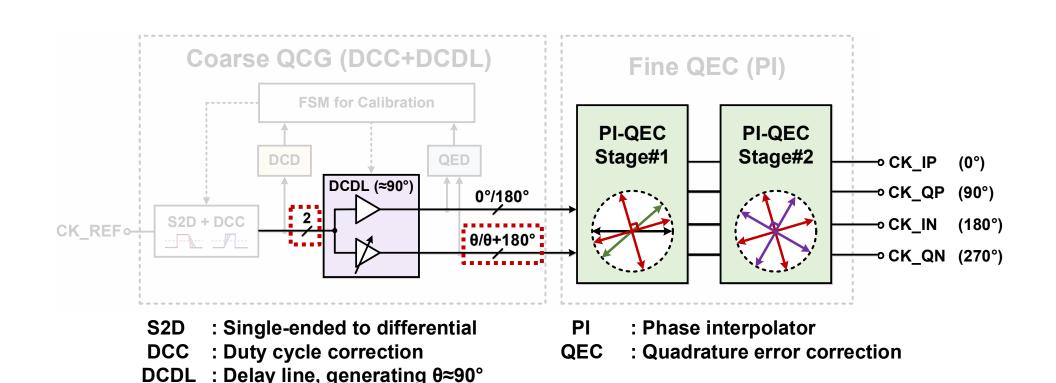- Is it good enough?
- Two major issues: duty cycle distortion and initial phase error




Proposed QCG: Duty Cycle Distortion-Concept

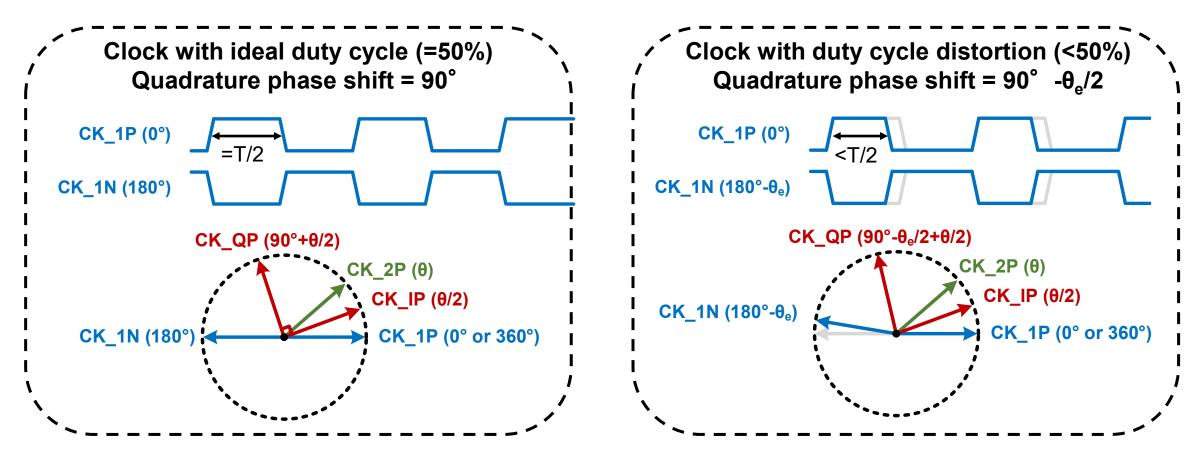Duty cycle distortion → Differential phase ≠ 180° → Generated quadrature phase shift ≠ 90°




Proposed QCG: Duty Cycle Distortion-Circuit

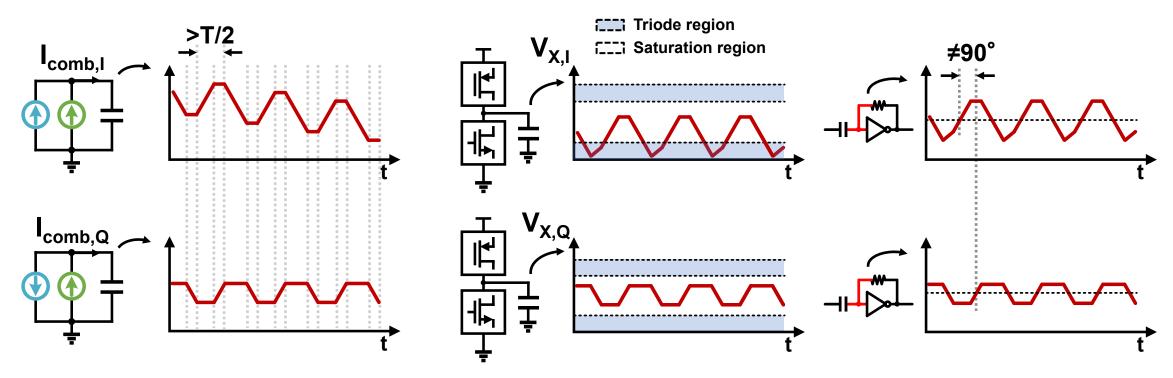- When duty cycle distortion exists in the input clocks:
 - Decreasing/increasing trend in the load voltage waveforms → push transistors into triode region



Proposed QCG: AM-PM of the C2C Converter

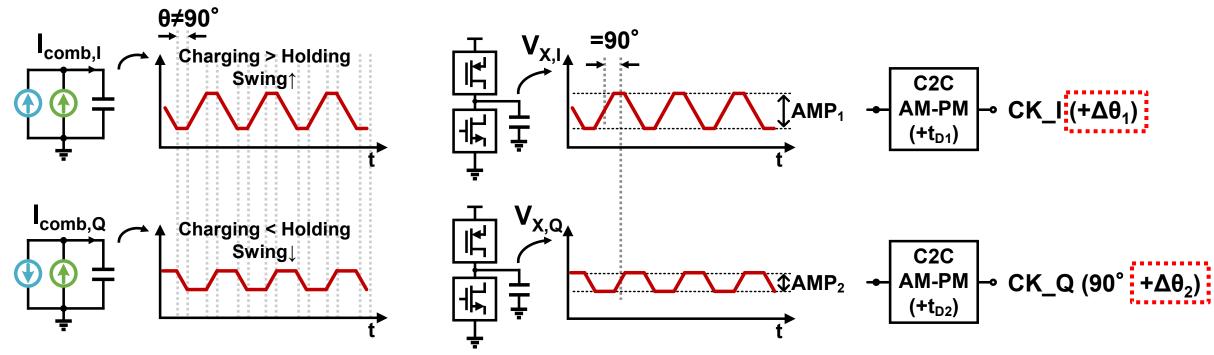
- \triangleright If initial phase shift θ significantly deviates from 90° :
 - Large swing difference of voltage waveforms (AMP₁ \neq AMP₂) \rightarrow skew induced by C2C AM-PM characteristics ($\theta_{D1} \neq \theta_{D2}$)



C2C: CML-to-CMOS Converter

Proposed QCG: Calibration

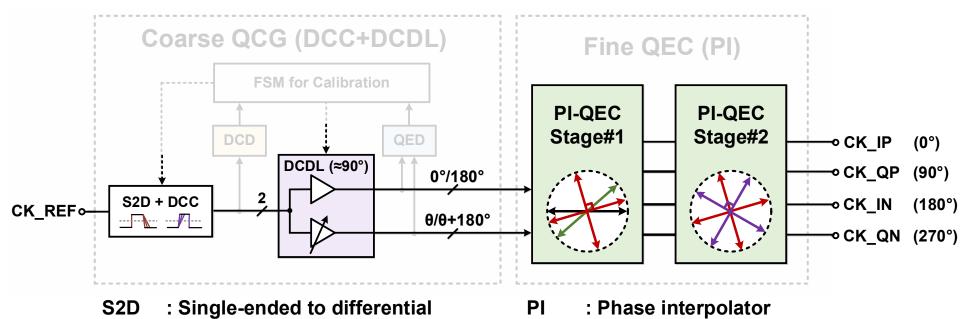- For optimal QCG performance, initial calibration is necessary
 - Duty cycle distortion from the input clocks
 - Quadrature delay generated by DCDL




DCC: Duty cycle correction

DCDL : Delay line, generating θ≈90°

QEC: Quadrature error correction


Proposed QCG: S2D and Duty Cycle Correction

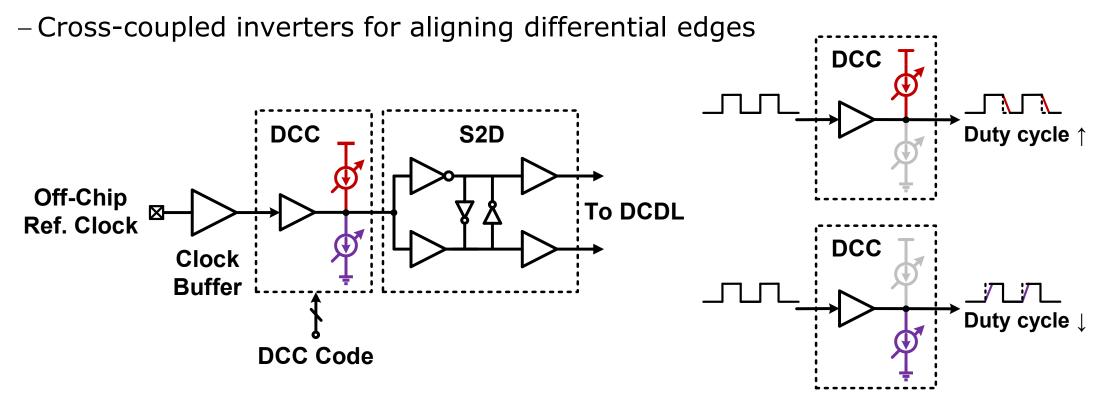- Single-ended duty cycle correction (DCC)
 - Pull-down/pull-up current modulating rising/falling transition time
- Single-ended-to-differential (S2D) converter



Proposed QCG: Calibration

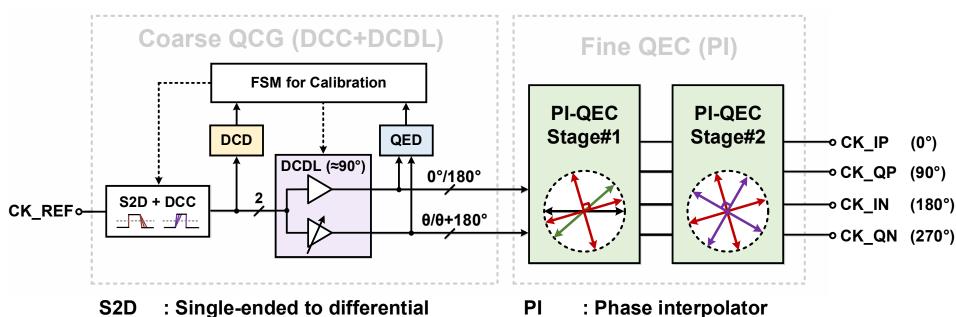- Digital automatic calibration scheme:
 - Error detection circuits (DCD, QED)
 - FSM for performing automatic calibration



QEC

: Single-ended to differential


DCC : Duty cycle correction

: Delay line, generating θ≈90°

: Quadrature error correction


Proposed QCG: Digital Calibration

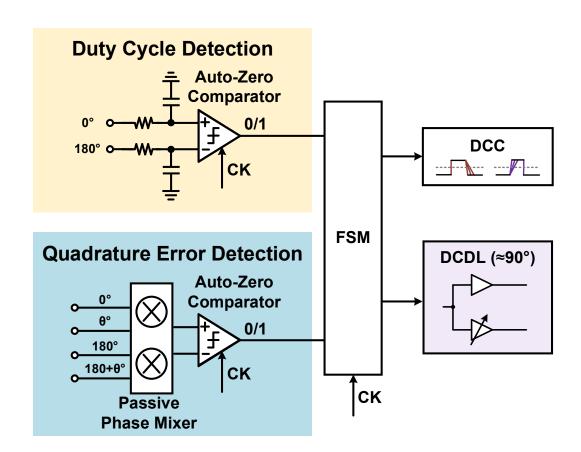Digital Calibration: error detection circuits + FSM




Proposed QCG: Duty Cycle Detection

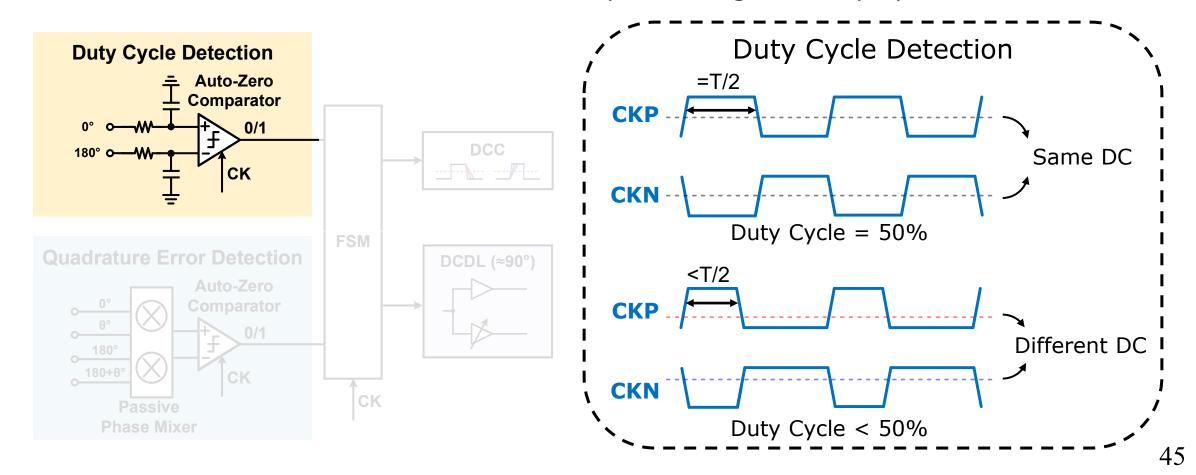- RC low-pass filters for duty cycle detection
 - extract DC levels of the P and N clock, representing the duty cycle




Proposed QCG: Duty Cycle Detection

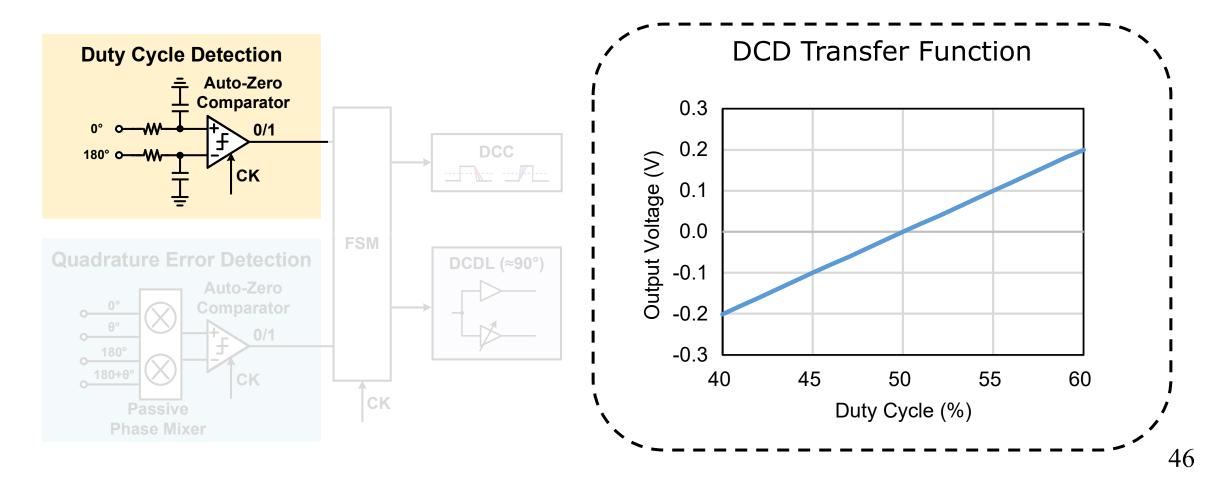RC low-pass filters for duty cycle detection: 20.1 mV/1%, zerocrossing point std. dev.: 8.2 mV




Proposed QCG: Quadrature Error Detection

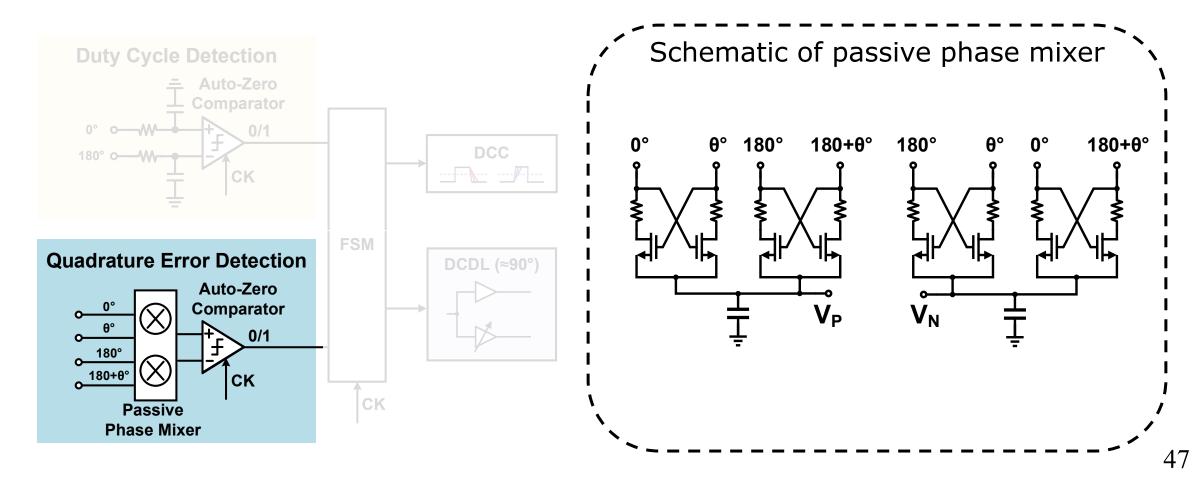A passive mixer (passive XOR) converts the quadrature error to DC voltage




Proposed QCG: Quadrature Error Detection

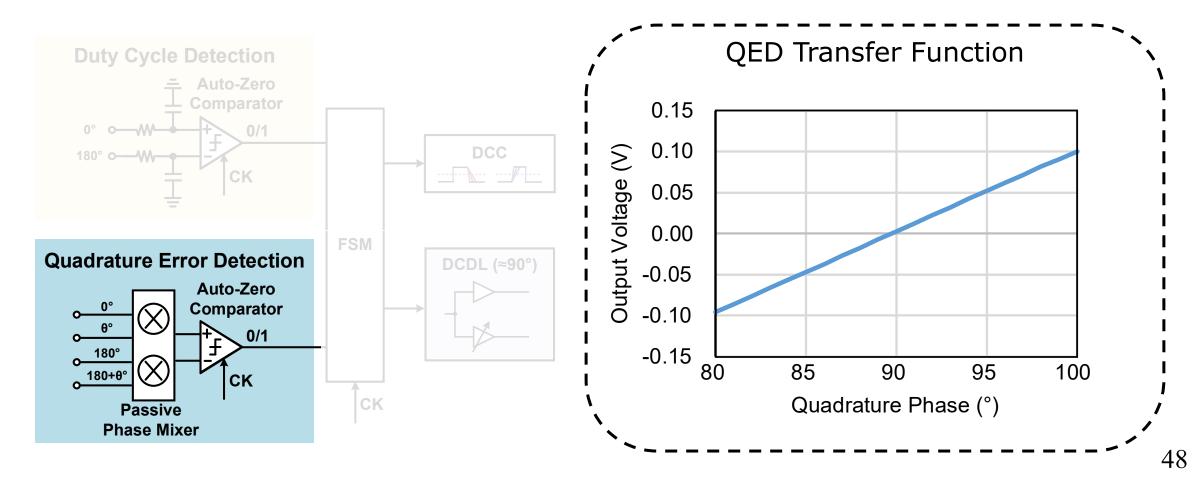A passive phase mixer (passive XOR) converts the quadrature error to DC voltage: 10.1 mV/°, zero crossing point std. dev.: 13.2 mV



Proposed QCG: Comparator

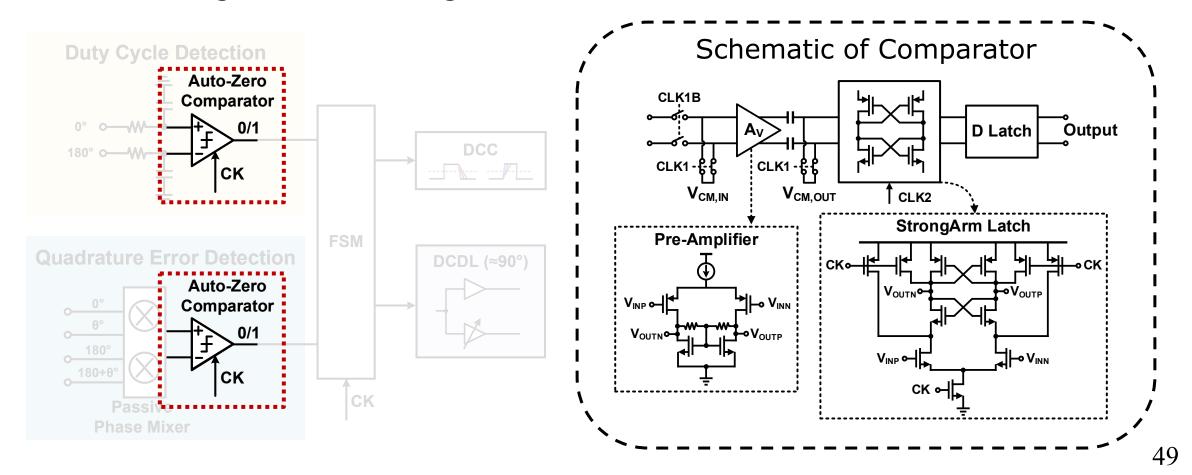- Comparators slice the detection output to digital "1" and "0"
 - -1: above target; 0: below target




Proposed QCG: Comparator

Comparator with offset cancellation


– Input offset standard deviation = 400 uV $_{rms}$ \sim 0.02% duty cycle and 0.04 $^{\circ}$

phase error

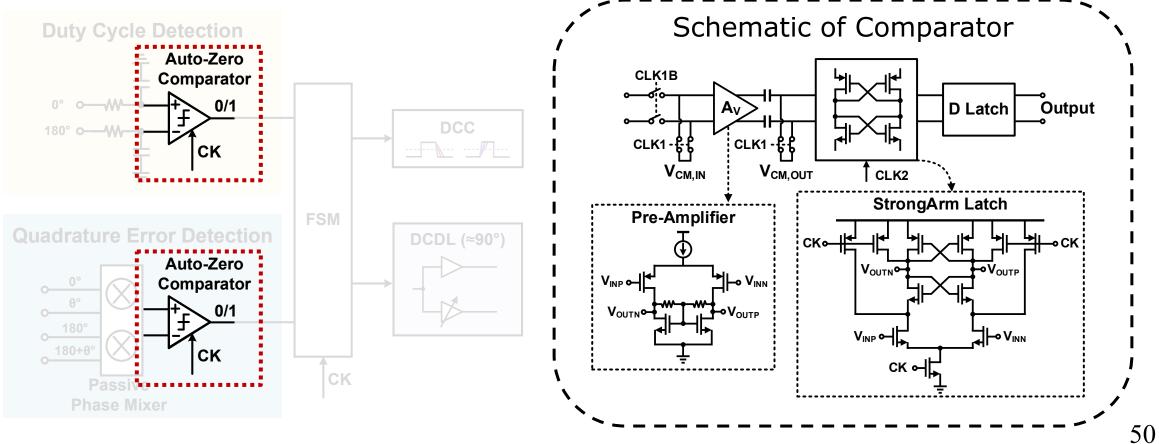

Proposed QCG: FSM

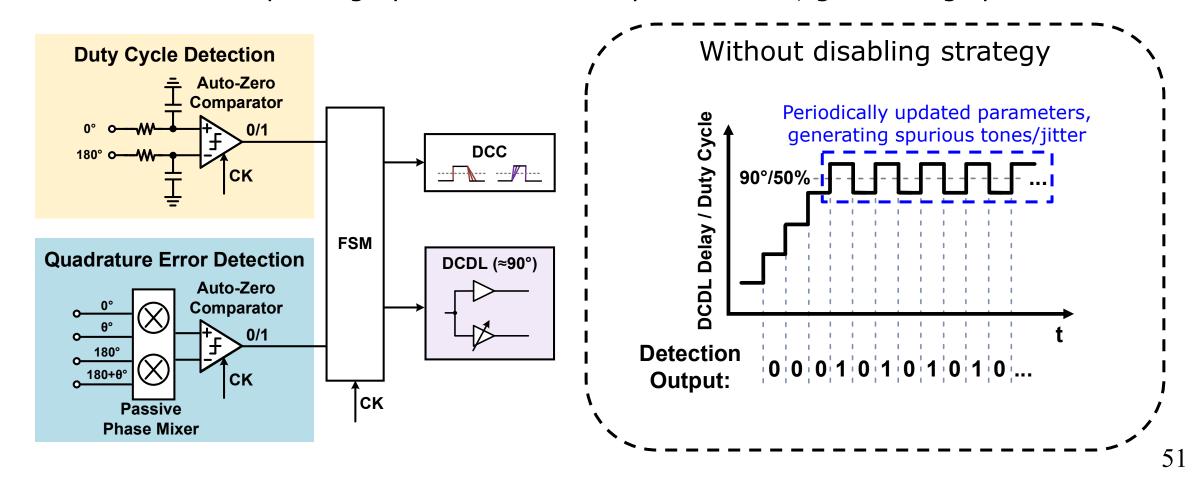- FSM without disabling strategy
 - Parameters keep being updated near the optimal value, generating spurs




Proposed QCG: FSM

FSM with a pattern-detecting disabling strategy


– Successive detection output are recorded; when it toggles between 1 and 0 for M

times, disable the calibration

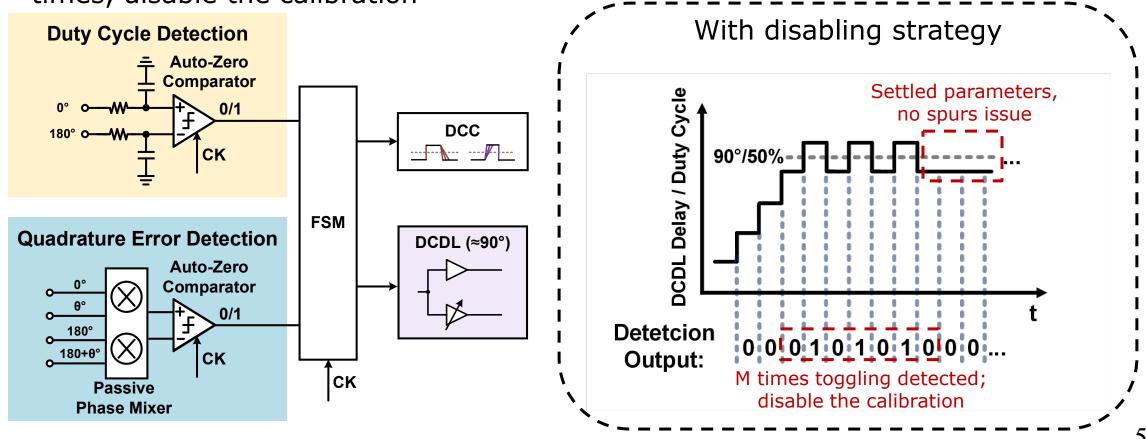

Proposed QCG: Design Summary

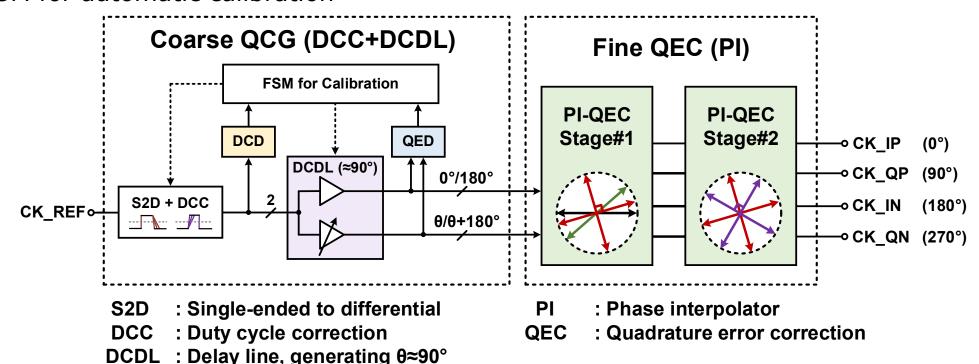- Proposed QCG system:
 - Duty cycle correction (DCC) to calibrate input duty cycle errors
 - A digital controlled delay line (DCDL) for generating coarse quadrature phase
 - A 2-stage open-loop quadrature error corrector (QEC) for reduce residual errors
 - FSM for automatic calibration




Outline

- Introduction
- Clocking in Wireline Systems
- Proposed QCG with Open-loop QEC
- Measurement Results
- Conclusion and Future Work


Measurement Result: Chip Micrograph

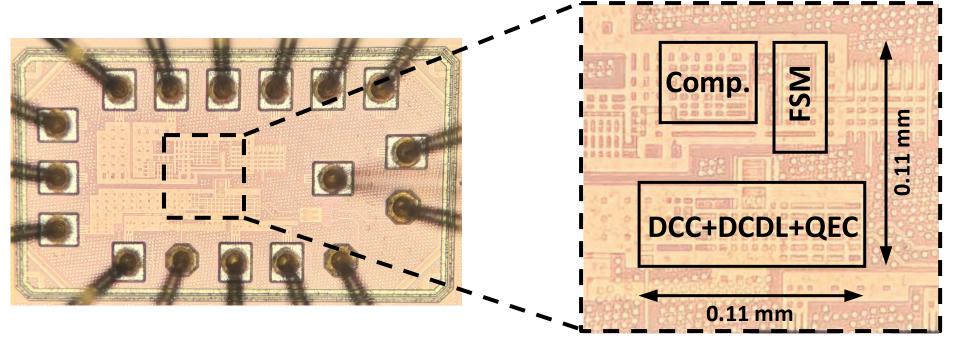- The prototype chip is fabricated in TSMC 28-nm CMOS technology
- Area: 12100 um² (with FSM and comparators), 3300 um² (core area excluding digital blocks)




Measurement Result: Setup

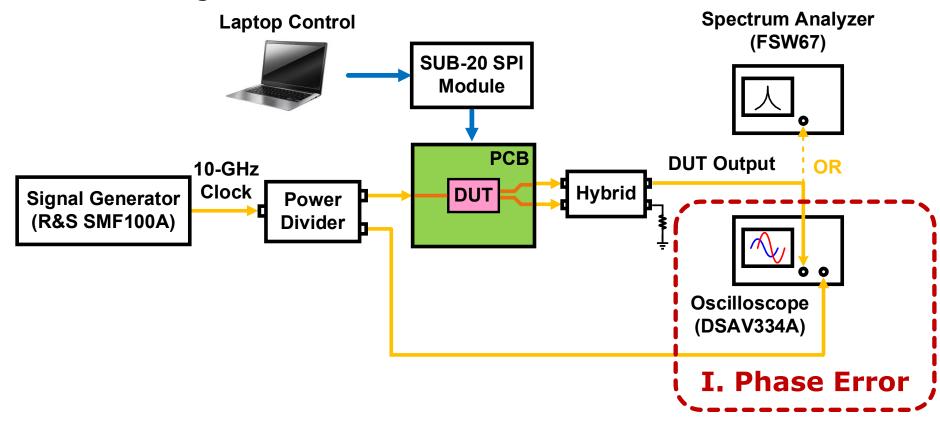
- Measurement setup:
 - Phase error testing
 - Phase noise testing



Measurement Result: Phase Accuracy

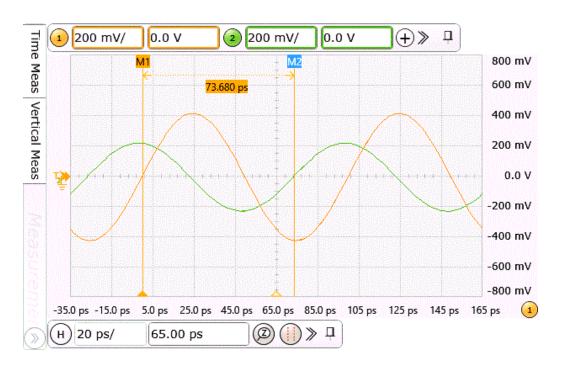
- Reference-to-I delay (t_{REF-I}) and reference-to-Q delay (t_{REF-Q}) are separately measured
- Quadrature phase delay t_{I-Q} = t_{REF-Q} t_{REF-I}



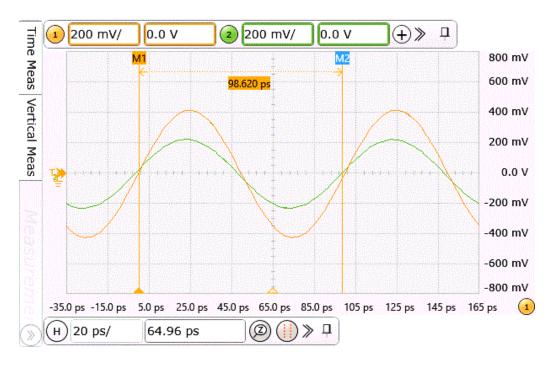


Measurement Result: Phase Accuracy

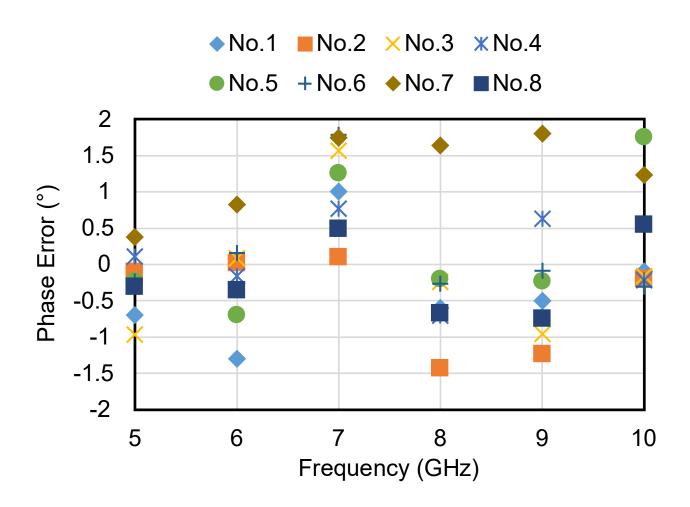Measured phase error ≤1.8° from 5-10 GHz across 8 chip samples




Measurement Result: Setup

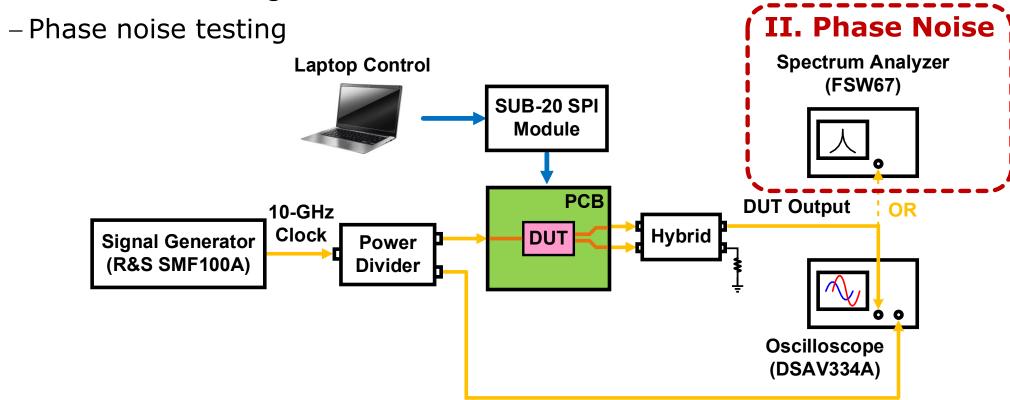- Measurement setup:
 - Phase error testing



Measurement Result: Phase Noise/RMS Jitter

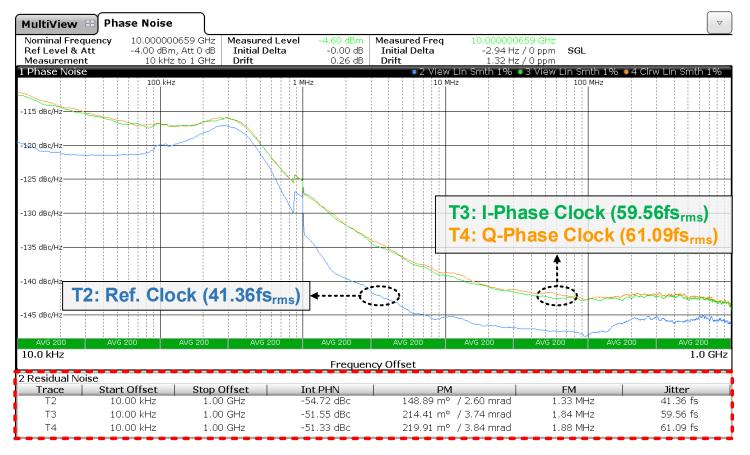
- Integrated jitter (10k-1GHz) = 61.09 fs (Q-Phase), 59.56 fs (I-Phase)
- Reference jitter = 41.36 fs_{rms} , calculated jitter contribution = 45 fs_{rms}



Measurement Result: Power Breakdown

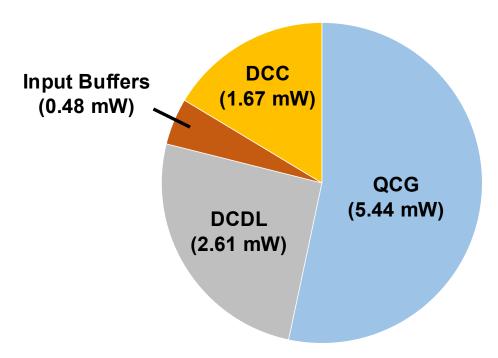- Total power consumption: 10.2 mW at 10-GHz operation
- Negligible digital power ~ 250 uW during calibration-active region





Comparison Table

Other open-loop methods

					,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,,		
	This work	Columbia JSSC'23 [1]	Columbia JSSC'22 [2]	Xilinx ISSCC'18 [3]	Intel ESSCIRC'16 [4]	UT Dallas CICC'11 [5]	IBM ISSCC'08 [6]
Architecture	Open-loop	DLL	DLL+IL-QLL	IL-QLL	Open-loop	Open-loop	Open-loop
Calibration	Digital Auto. Calibration	Manual	Manual	Frequency track loop	Digital Auto. Calibration	None	None
Number of phases	4	4	8	8	4	8	4
Process	28nm CMOS	65nm CMOS	65nm CMOS	7nm FinFET	28nm CMOS	65nm CMOS	65nm CMOS
Frequency Range (GHz)	5-10	3.5~11	5~8	4~16	1~2.6	8~12	0.37~2.5
Power (mW)	10.2 @10 GHz	7.8 @7GHz	15.6 @7GHz	10 @16GHz	4.4 @2GHz	14.8 @10GHz	2.6 @2.5GHz
Power Efficiency (mW/GHz)	1.02	1.11	2.23	0.63	2.2	1.48	1.04
Jitter (fs, _{rms})	62.1 @10 GHz	48.1 @7 GHz	65.2 @7 GHz	80 @16 GHz	37.6	470 @10GHz	N/A
Integration Band (Hz)	10k-1G	10k-1G	10k-1G	100k-1G	10k-100M	N/A	N/A
IQ Error (°)	≤1.8	≤0.9	≤0.5	≤1	≤5	≤3.1	≤5
Area(um²)	12100	12000	21000	N/A	3000	1500	500
Supply (V)	0.9	1.2	1.2	1.2/0.88	1.1	1.1	1

Outline


- Introduction
- Clocking in Wireline Systems
- Proposed QCG with Open-loop QEC
- Measurement Results
- Conclusion and Future Work

Conclusion

- A QCG featuring DCC, DCDL, open-loop QEC and digital automatic calibration is proposed
- The design provides an open-loop alternative of generating quadrature clocks and correcting residual phase error
- The design is verified by simulation and measurement, demonstrating a good performance in power, jitter, phase accuracy and operation range

Future Work

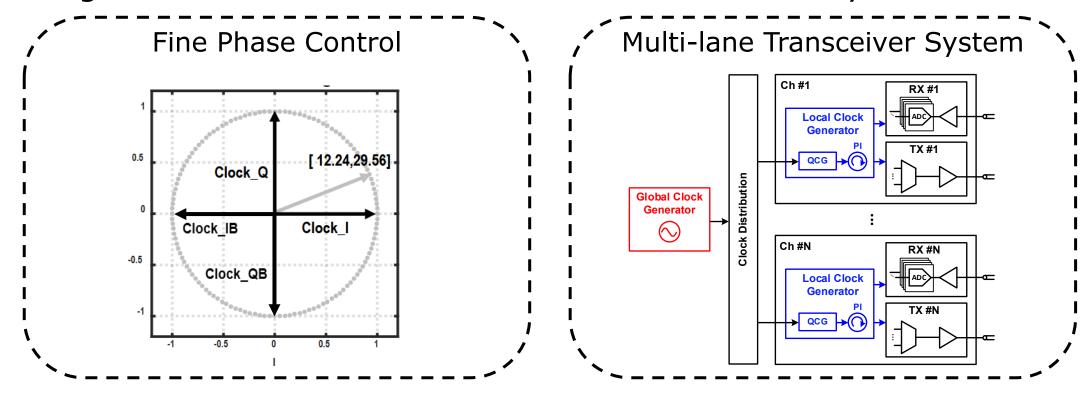- Fine phase control from 0 to 360° using quadrature clocks as the reference
 - de-skewing, alignment, clock & data recovery (CDR)
- Integration with the overall multi-lane transceiver system



Publication

Conference

 Shaokang Zhao, Li Wang, and C. Patrick Yue, "Design of A 5–10 GHz Open-Loop Quadrature Clock Generator for High-Speed Wireline Systems (under review)," in 2025 IEEE 23rd Interregional NEWCAS Conference, 2025.

Journal

- Shaokang Zhao, Li Wang, and C. Patrick Yue, "A 5-10 GHz Quadrature Clock Generator with Open-loop Quadrature Error Correction in 28-nm CMOS (under review)," IEEE Solid-State Circuits Letters, 2025.

Reference

- [1] Toprak-Deniz et al., "A 128-Gb/s 1.3-pJ/b PAM-4 Transmitter With Reconfigurable 3-Tap FFE in 14-nm CMOS," in IEEE Journal of Solid-State Circuits, vol. 55, no. 1, pp. 19-26, Jan. 2020.
- [2] Z. Wang and P. R. Kinget, "A 65nm CMOS, 3.5-to-11GHz, Less-Than 1.45LSB-INLpp, 7b Twin Phase Interpolator with a Wideband, Low Noise Delta Quadrature Delay-Locked Loop for High-Speed Data Links," 2022 IEEE International Solid-State Circuits Conference (ISSCC), San Francisco, CA, USA, 2022, pp. 292-294.
- [3] K. -h. Kim, P. W. Coteus, D. Dreps, S. Kim, S. V. Rylov and D. J. Friedman, "A 2.6mW 370MHz-to-2.5GHz Open-Loop Quadrature Clock Generator," 2008 IEEE International Solid-State Circuits Conference Digest of Technical Papers, San Francisco, CA, USA, 2008, pp. 458-627.
- [4] Z. Zhang, G. Zhu, C. Wang, L. Wang and C. P. Yue, "A 32-Gb/s 0.46pJ/bit PAM4 CDR Using a Quarter-Rate Linear Phase Detector and a Self-Biased PLL-Based Multiphase Clock Generator," in IEEE Journal of Solid-State Circuits, vol. 55, no. 10, pp. 2734-2746, Oct. 2020.
- [5] S. Chen et al., "A 4-to-16GHz inverter-based injection-locked quadrature clock generator with phase interpolators for multi-standard I/Os in 7nm FinFET," 2018 IEEE International Solid-State Circuits Conference (ISSCC), San Francisco, CA, USA, 2018, pp. 390-392.

Reference

[6] Z. Wang, Y. Zhang, Y. Onizuka and P. R. Kinget, "11.4 A High-Accuracy Multi-Phase Injection-Locked 8-Phase 7GHz Clock Generator in 65nm with 7b Phase Interpolators for High-Speed Data Links," 2021 IEEE International Solid-State Circuits Conference (ISSCC), San Francisco, CA, USA, 2021, pp. 186-188.

[7] A. K. Mishra, Y. Li, P. Agarwal and S. Shekhar, "A 9b-Linear 14GHz Integrating-Mode Phase Interpolator in 5nm FinFET Process," 2022 IEEE International Solid-State Circuits Conference (ISSCC), San Francisco, CA, USA, 2022, pp. 1-3.

Acknowledgement

This work was supported in part by the Areas of Excellence Scheme of Hong Kong, under the grant AoE/E601/22-R, in part by the General Research Fund of Hong Kong, under the grant no.16205522 and no.16205023

Acknowledgement

- Prof. C. Patrick Yue
- Prof. Wing Hung Ki and Prof. Fengbin Tu
- Groupmates from OWL
- My parents and my friends
- All the audience today






Thanks!

Optical Wireless Lab


Department of Electronic and Computer Engineering

The Hong Kong University of Science and Technology (HKUST)


Proposed QCG: Duty Cycle Self Correction

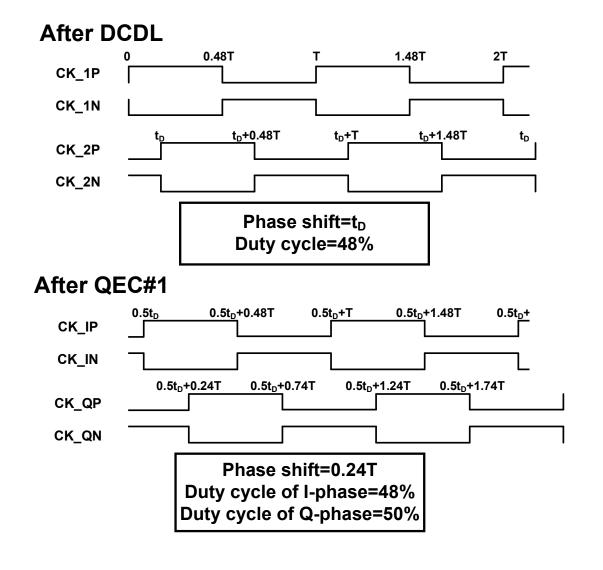



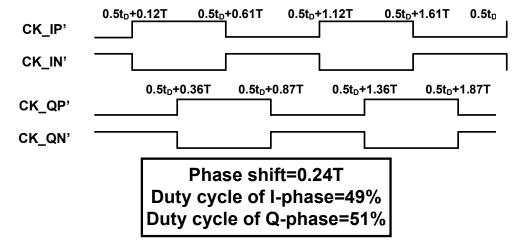


After QEC#3

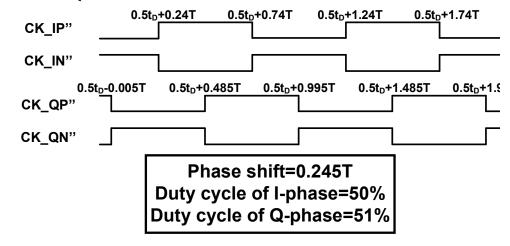


Proposed QCG: Duty Cycle Self Correction


After QEC#2

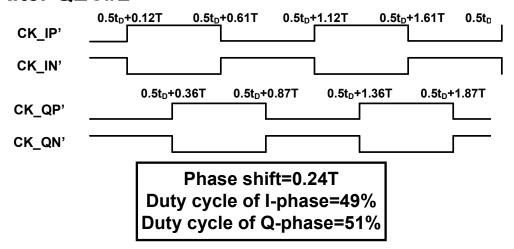

After QEC#3

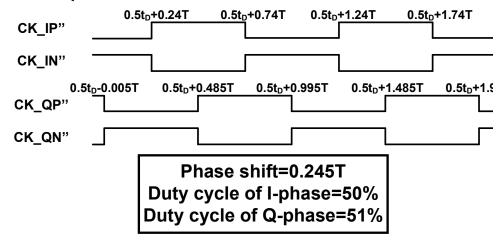



After QEC#4

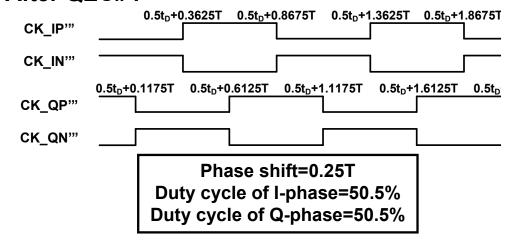

Proposed QCG: Digitally Controlled Delay Line

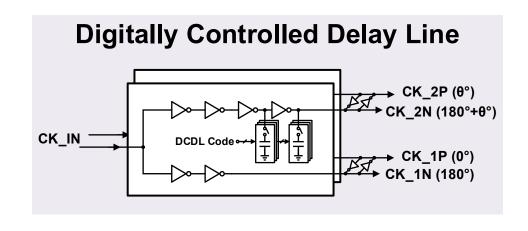
> ~1.2-ps step (5.4° for 10 GHz), 19.2-ps range




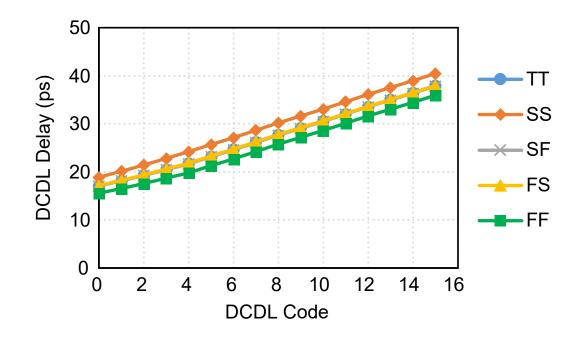

Proposed QCG: Duty Cycle Correction

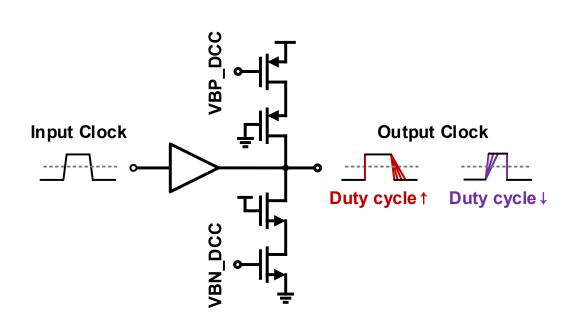- Current mirror to modulate pull-up and pull-down strength
- Binary-implemented current segments for digital control




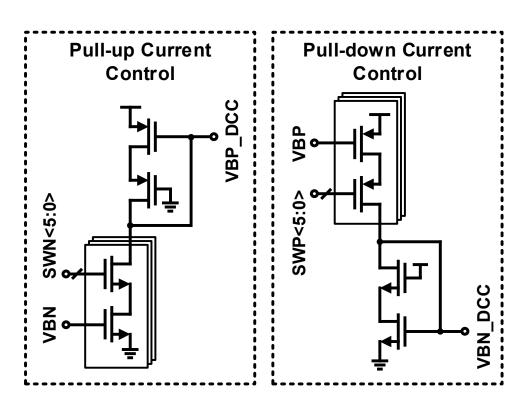

8/19/2025


Proposed QCG: Duty Cycle Correction

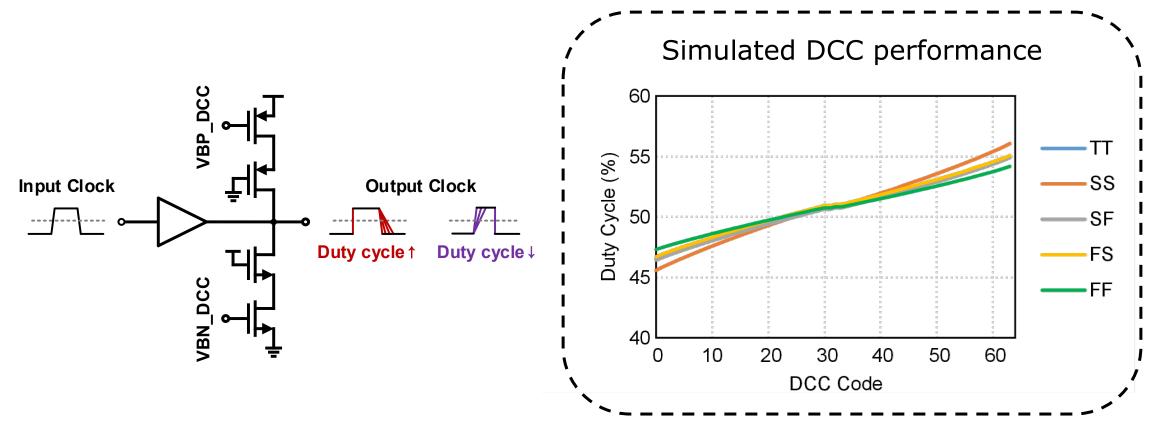▶ Simulated DCC performance: ~0.13-% step, ~8.5-% range (TT)




Proposed QCG: Duty Cycle Distortion-1

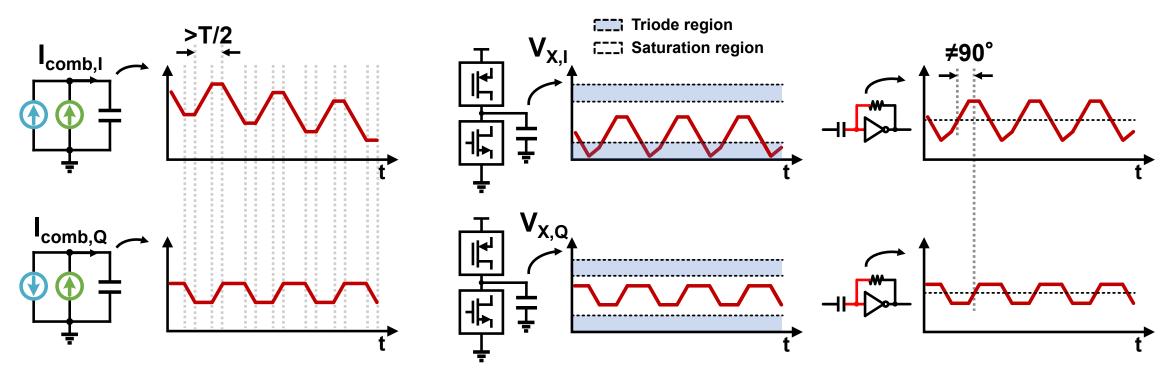- When duty cycle distortion exists in the input clocks:
 - Decreasing/increasing trend in the load voltage waveforms → push transistors into triode region




Proposed QCG: Duty Cycle Distortion-2

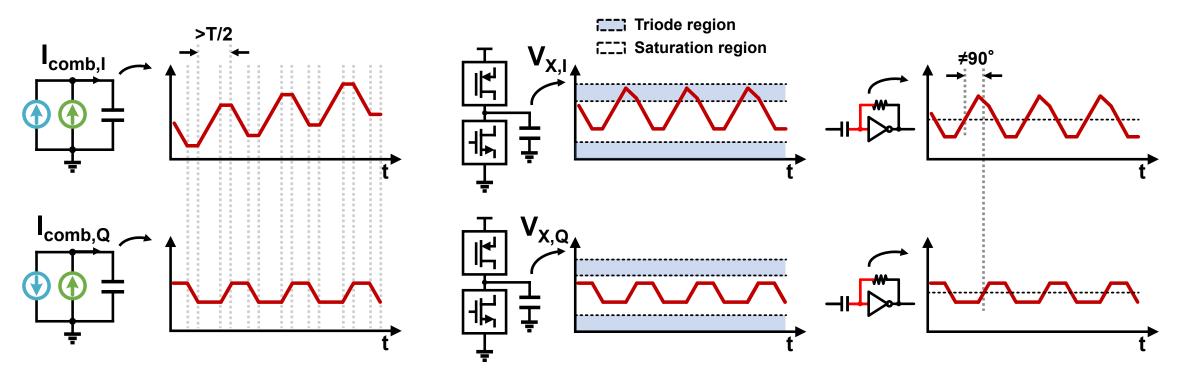
- When duty cycle distortion exists in the input clocks:
 - Decreasing/increasing trend in the load voltage waveforms → push transistors into triode region



Proposed QCG: Current mismatch

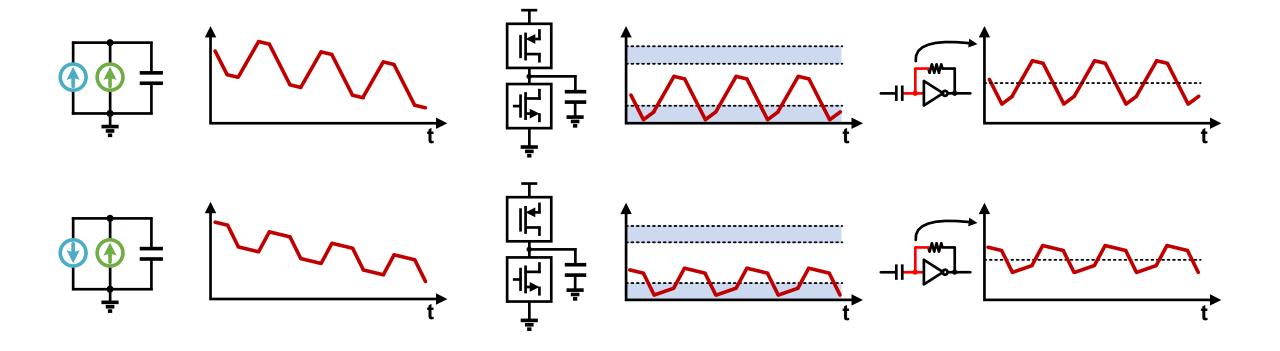

Proposed QCG: Large Current

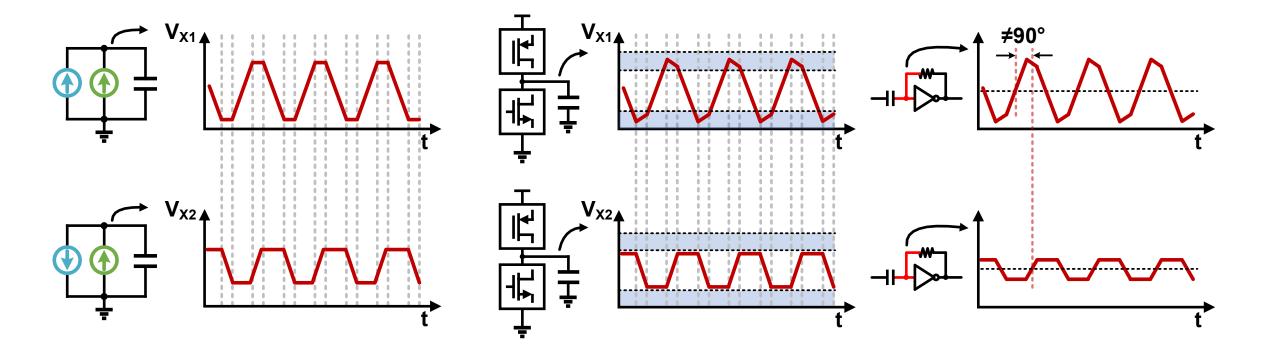

Proposed QCG:

Layout implementation

